

Integrated Circuit Design

Homework #1

Due: 2020/04/29 13:00 (No late homework is allowed.)

1. Setup HSPICE following the steps listed in [20200408_T1_Linux_and_Hspice.pdf](#).
2. Use [mosistsmc180.sp](#) as the transistor model.
3. Write a SPICE deck for NAND2 using `.subckt` . Save it in Plain Text format using the name [nand2.sp](#) .
4. Write a SPICE deck for a multiplexer ($D = D_0\bar{S} + D_1S$) using three NAND2 gates.
5. Run HSPICE using the deck prepared in Step 4. Test all possible output cases:
(D_0, D_1, S) = (0, 0, 0), (0, 0, 1), (0, 1, 0), (0, 1, 1), (1, 0, 0), (1, 0, 1), (1, 1, 0), (1, 1, 1).
6. Use COSMOS scope to show the results in Step 5.
7. Take a snapshot of the screen showing the waveforms in Step 5.
8. Paste the snapshot taken above in a document. Save this document in PDF format using the name, [multiplexer_wfs.pdf](#).
9. Save the SPICE deck in Plain Text format using the name, [multiplexer.sp](#) .
10. Create a directory named [~/ICD2020/HW1](#) and put the above three files under the directory.
11. Compress the directory use the following command:
[tar cvzf YourID#_HW1.tar.gz HW1](#)
12. Submit your [YourID#_HW1.tar.gz](#) file to ceiba.